

# Basic Electricity 2

ME 120 Lecture Notes

Portland State University

Mechanical and Materials Engineering


# Learning Objectives

Successful completion of this module will enable students to

- Compute power dissipation in simple DC circuits, using Ohm's law
- Combine resistors in series to obtain one equivalent resistor
- Combine resistors in parallel to obtain one equivalent resistor
- Reduce resistor networks to an equivalent resistance
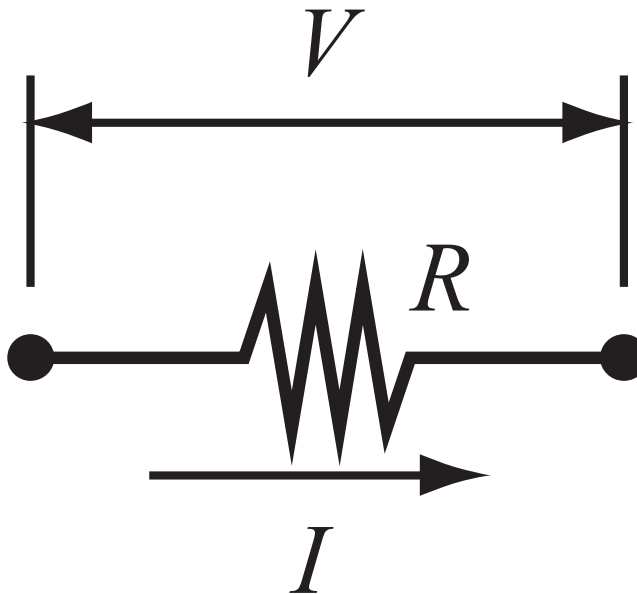
# Review

Ohm's law relates voltage, current and resistance for the flow of current through a conductor.



$$V = I \times R$$

in amp (A)

in volts (V)

in ohms ( $\Omega$ )

# Definition

## ***Power:***

Power is the rate at which work is done. It is also the rate at which energy is expended.

$$P = \frac{\text{Work}}{\text{time}} = \frac{\text{Energy}}{\text{time}}$$


in watts (W)

in joules (J)

in seconds (s)

# Power

For electrical current:

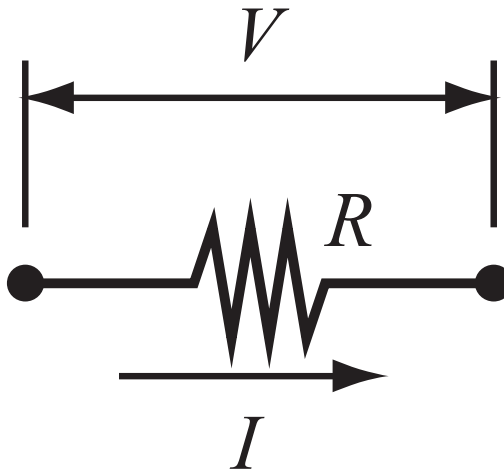

$$P = V \times I$$

Using Ohm's Law:

$$P = V \times I = (IR) \times I = I^2 R$$

$$P = V \times I = V \times \frac{V}{R} = \frac{V^2}{R}$$

Ohm's Law:

$$V = I \times R$$

$$I = V / R$$


# Power Limits

All electrical devices have limits on the power they can handle

Too much power consumption will cause a device to fail or “burn out”

We need to work within the power limits when we design equipment

# Characteristics of a light bulb

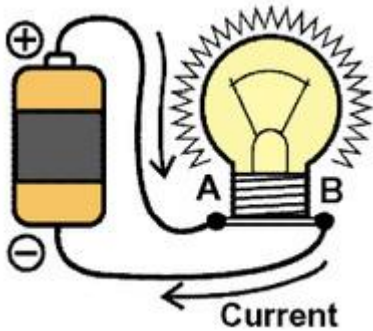


## Given:

- Battery voltage:  $V_b = 1.5 \text{ V}$
- Current going through the light bulb is  $I = 2 \text{ A}$

## Find:


- What is  $R$ , resistance of light bulb
- What is  $P$ , power dissipated by the light bulb

# Characteristics of a light bulb

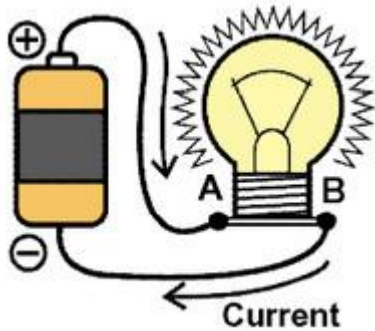
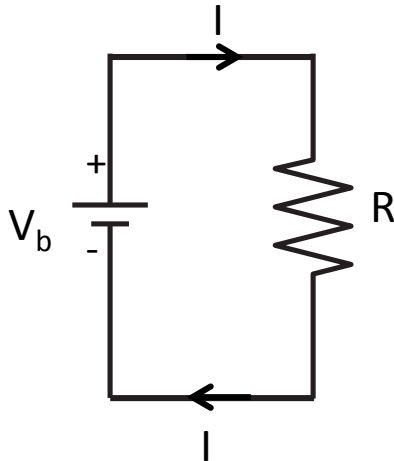
## Given:

- Battery voltage:  $V_b = 1.5 \text{ V}$
- Current going through the light bulb is  $I = 2\text{A}$







## Results:

- Resistance  $R = V_b / I = 0.75 \Omega$
- Power is  $P = V_b I = 3\text{W}$ .



# Two light bulbs

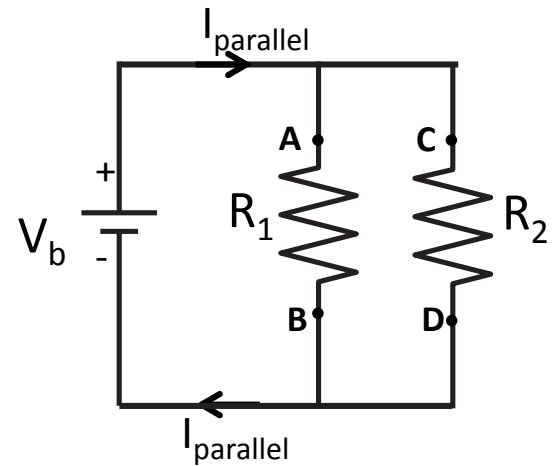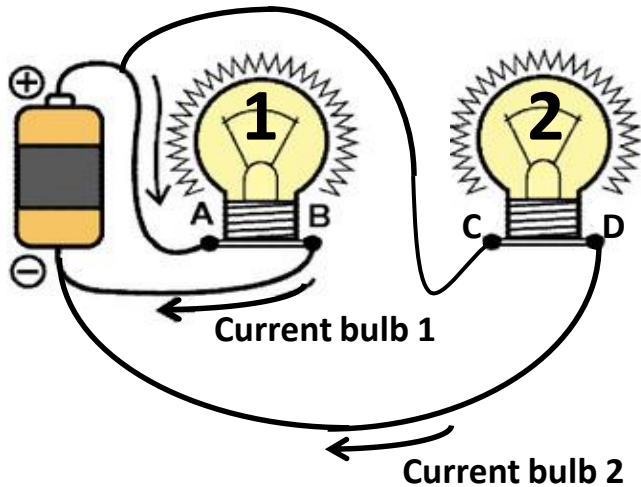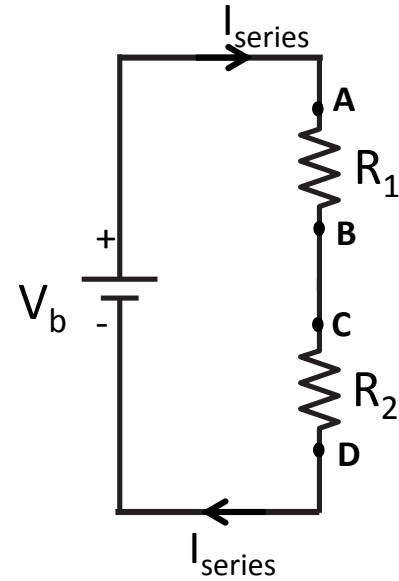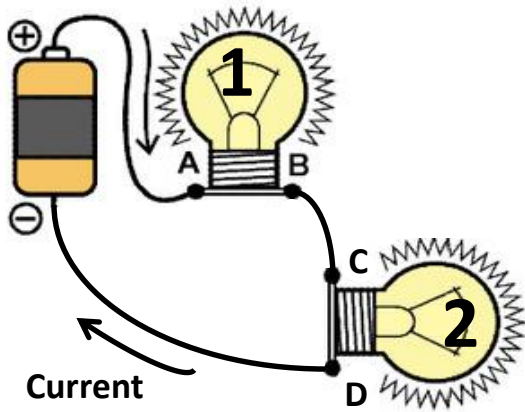


# Equivalent Resistance

Most interesting and useful circuits are a combination of individual components
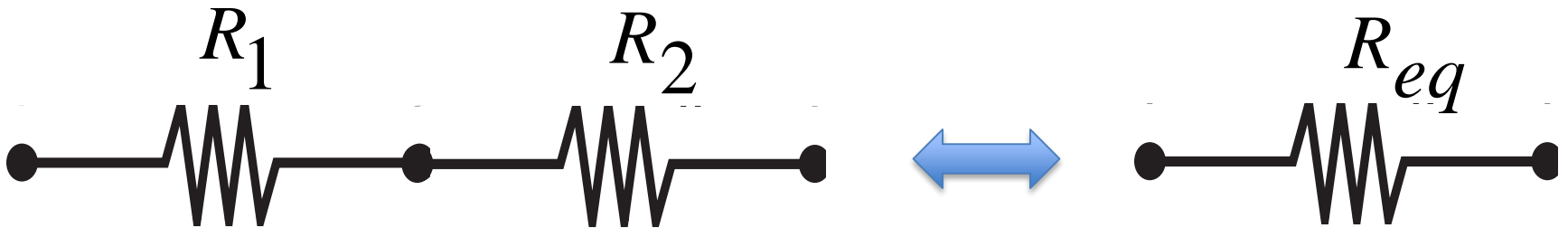
## ***Resistors in Series***

Resistors in series are equivalent to a single resistor having a resistance equal to the sum of the individual resistors.




$$R_{eq\_series} = R_1 + R_2$$

# Equivalent Resistance

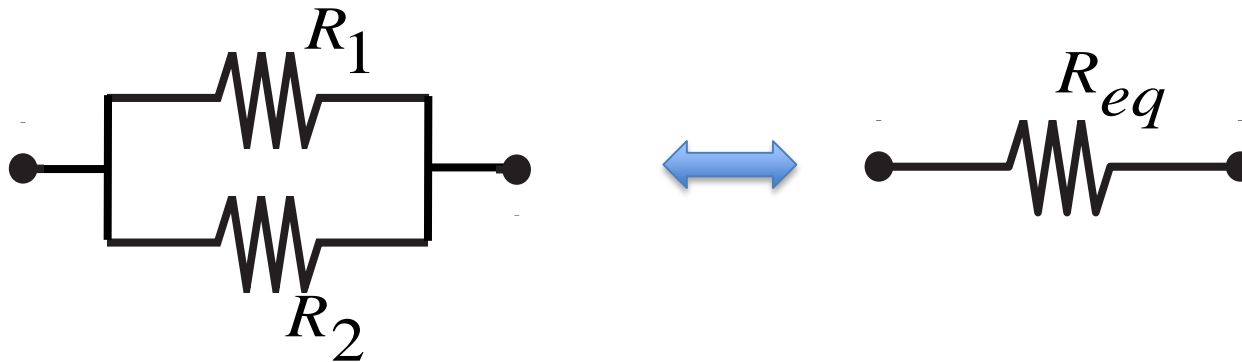
## ***Resistors in Parallel***

Resistors in parallel are equivalent to a single resistor having a value obtained by summing the inverse of the individual resistors.




$$\frac{1}{R_{eq\_parallel}} = \frac{1}{R_1} + \frac{1}{R_2} \quad \text{or} \quad R_{eq\_parallel} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}$$

# Two light bulbs

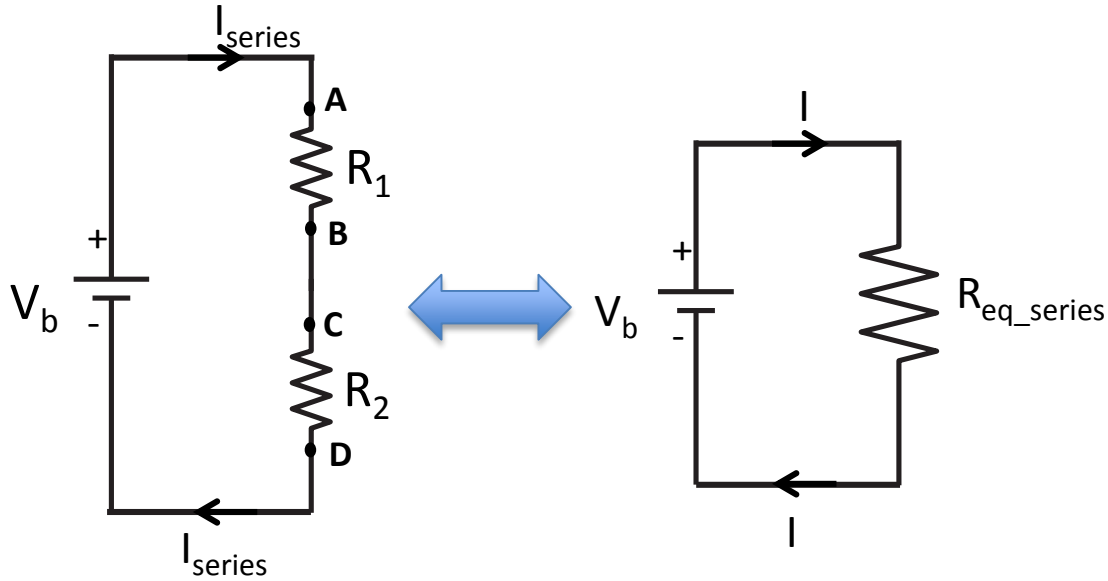

$$P_{series} = \frac{V_b^2}{2R_1}$$

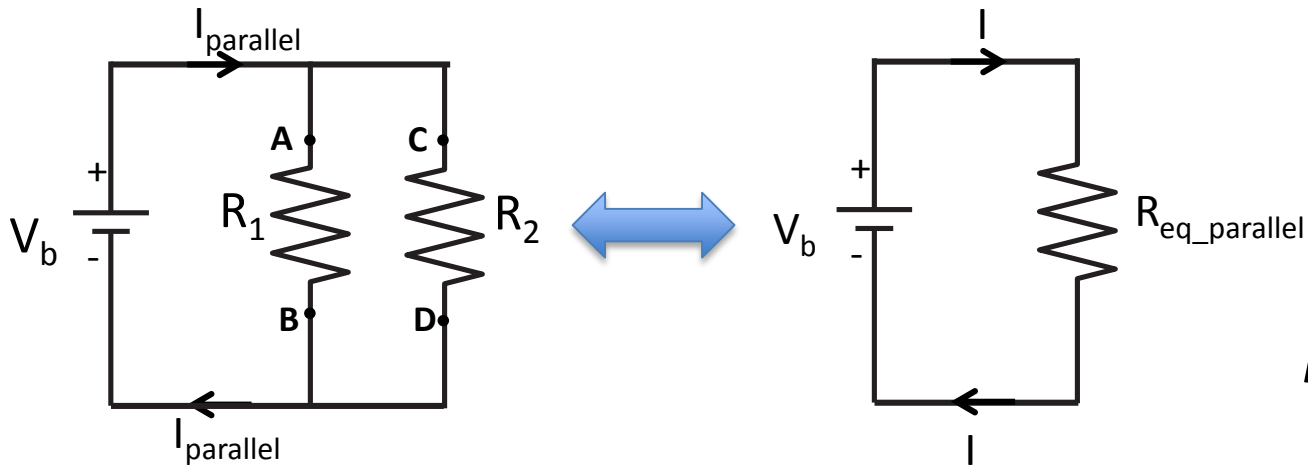

$$P_{parallel} = \frac{2V_b^2}{R_1}$$

The end 😊

Thank you!