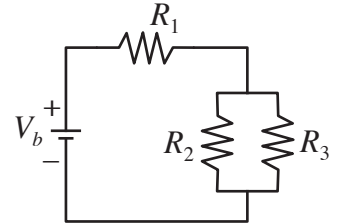


Simplifying Circuits with Multiple Resistors


The example problems provided here do not have numerical values specified for the battery voltage (V_b) or the resistors (R_1, R_2, \dots). The goal of these exercises is to focus on a procedure for simplifying arrangements of resistors, without being limited by any one set of numerical values.

1. For the circuit in the sketch to the right
 - a. How much current is supplied by the battery?
 - b. How much power is dissipated by the circuit?
 - c. How much power is dissipated by R_1 ?




Assume that numerical values of V_b and all resistances are known. The goal of the exercise is to obtain an algebraic expression that answers each of the questions.

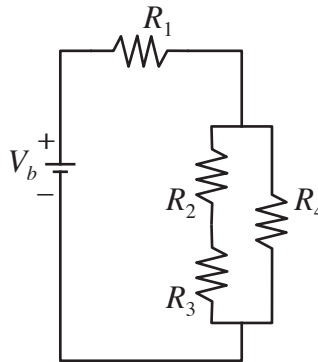2. Answer the questions raised in item 1 for the circuit shown below.



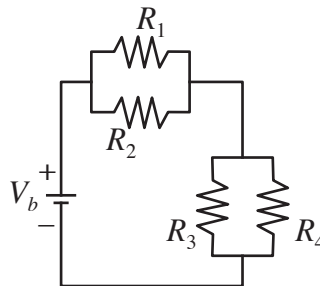3. Answer the questions raised in item 1 for the circuit shown below.




Solutions to Practice Problems

Simplifying Circuits with Multiple Resistors

The analysis of problems 1 through 3 follows these main steps:

- Use rules for resistors in parallel and resistors in series to obtain an equivalent resistance, R_{eq} . With R_{eq} known, apply Ohm's law to compute I_{tot} from $V_b = I_{\text{tot}}R_{\text{eq}}$, where I_{tot} is the current supplied by the battery.
- Compute the total power dissipated by the circuit with $P_{\text{tot}} = I_{\text{tot}}^2R_{\text{eq}}$ or $P_{\text{tot}} = V_bI_{\text{tot}}$ or $P_{\text{tot}} = V_b^2/R_{\text{eq}}$.
- Compute P_1 in one of two ways
 - Determine the current flowing through R_1 and compute $P_1 = I_1^2R_1$, or
 - Determine the voltage across R_1 and compute $P_1 = V_1^2/R_1$.

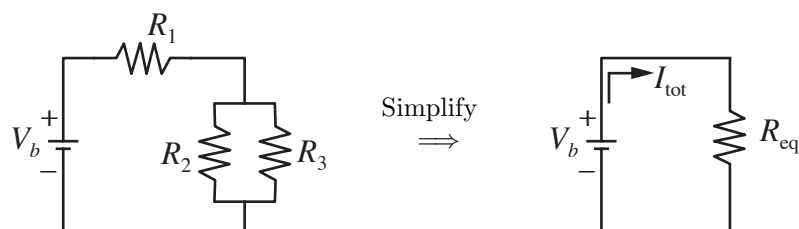- The circuit to be analyzed is shown below left. The first step of the analysis is to compute R_{eq} to obtain the equivalent circuit to the right.



- Compute the total current supplied by the battery.


Step 1: Obtain a formula for the equivalent resistance, R_{eq} of the entire circuit, by replacing combinations of two (or more) resistors with an equivalent resistance. The process is repeated until there is only one equivalent resistance remaining.

R_2 and R_3 are in parallel and can be combined into an equivalent resistance R_{23}

$$\frac{1}{R_{23}} = \frac{1}{R_2} + \frac{1}{R_3}$$

or, with algebraic rearrangement

$$R_{23} = \frac{R_2R_3}{R_2 + R_3}$$

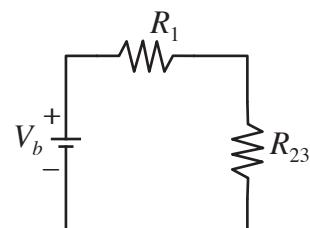


R_1 and R_{23} are in series and can be combined into an equivalent resistance R_{123} . Since R_{123} is the only remaining resistance, it is also R_{eq} for the entire circuit, i.e., $R_{123} = R_{\text{eq}}$.

$$R_{123} = R_{\text{eq}} = R_1 + R_{23}$$

Substituting the formula for R_{23} , gives
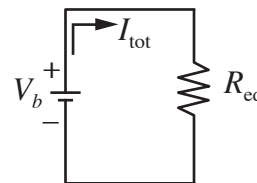
$$R_{\text{eq}} = R_1 + \frac{R_2 R_3}{R_2 + R_3} \quad (*)$$



The battery performs as if the three resistors in the given circuit are replaced by a single resistor with a resistance value of R_{eq} .

Step 2: Compute the total current leaving the battery.

Ohm's law for the equivalent circuit is

$$V_b = I_{\text{tot}} R_{\text{eq}}$$

Therefore, since V_b and R_{eq} are known

$$I_{\text{tot}} = \frac{V_b}{R_{\text{eq}}} \quad (**)$$

This concludes part (a) of the assignment. Note that it is possible to substitute the detailed formula for R_{eq} in the preceding expression.

$$I_{\text{tot}} = \frac{V_b}{R_1 + \frac{R_2 R_3}{R_2 + R_3}}$$

However, this more complicated formula is cumbersome and adds little insight into the solution. If the values of R_1 , R_2 and R_3 were known, then it would be better to compute R_{eq} as a numerical value from Equation (*), above, and then use that numerical value in Equation (**).

- b. The power dissipated by the entire circuit can be computed from any of these formulas.

$$P_{\text{tot}} = I_{\text{tot}}^2 R_{\text{eq}} \quad \text{or} \quad P_{\text{tot}} = V_b I_{\text{tot}} \quad \text{or} \quad P_{\text{tot}} = \frac{V_b^2}{R_{\text{eq}}}.$$

From the givens, V_b and all the resistance values are known. From the analysis of part (a), R_{eq} is known. Thus, at this point in the analysis, all three of the formulas for P_{tot} can be computed directly.

- c. The power dissipated by R_1 can be computed from any one of these formulas

$$P_1 = I_1^2 R_1 \quad \text{or} \quad P_1 = V_1 I_1 \quad \text{or} \quad P_1 = \frac{V_1^2}{R_1}.$$


Note that additional work would be required to find V_1 . Since R_1 is in series with the battery,

$$I_1 = I_{\text{tot}} \quad \text{therefore,} \quad P_1 = I_{\text{tot}}^2 R_1$$

Also note that the preceding formula for P_1 *only* applies to the circuit being analyzed in this problem. $P_1 = I_{\text{tot}}^2 R_1$ is not true for all circuits because in general $I_1 \neq I_{\text{tot}}$.

————— ◇ —————

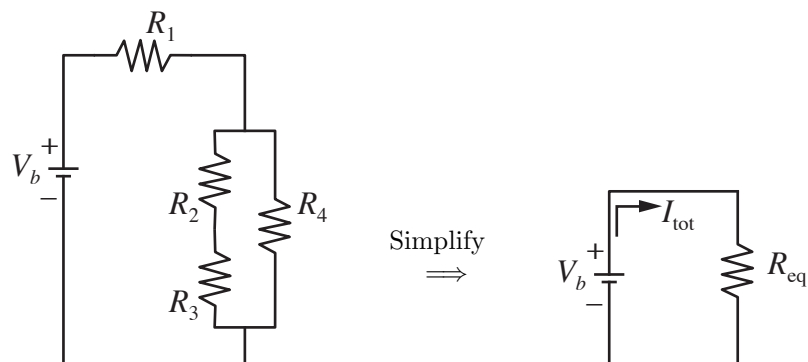2. The circuit to be analyzed is shown below left. The first step of the analysis is to compute R_{eq} to obtain the equivalent circuit to the right.



The steps are the same as in the preceding exercise. However, since the arrangement of resistances is different, the formula for R_{eq} will be different.


- a. Compute the total current supplied by the battery.

Step 1: Obtain a formula for the equivalent resistance, R_{eq} of the entire circuit.

R_2 and R_3 are in series and can be combined into an equivalent resistance R_{23}

$$R_{23} = R_2 + R_3$$

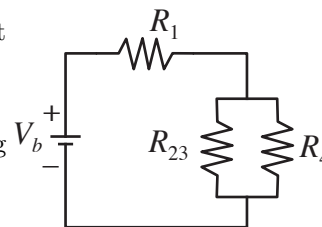Note that this is *not* the same R_{23} formula from the preceding exercise.




R_{23} and R_4 are in parallel and can be combined into an equivalent resistance R_{234}

$$\frac{1}{R_{234}} = \frac{1}{R_{23}} + \frac{1}{R_4}$$


or, with algebraic rearrangement
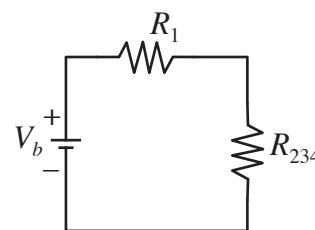
$$R_{234} = \frac{R_{23}R_4}{R_{23} + R_4}$$



R_1 and R_{234} are in series and can be combined into an equivalent resistance R_{1234} . Since R_{1234} is the only remaining resistance, it is also R_{eq} for the entire circuit, i.e., $R_{1234} = R_{\text{eq}}$.
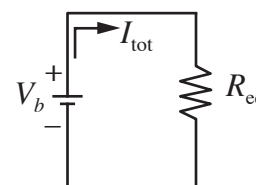
$$R_{1234} = R_{\text{eq}} = R_1 + R_{234}$$



It's possible to substitute the definitions of R_{234} and R_{23} into the expression for R_{eq}

$$R_{\text{eq}} = R_1 + R_{234} = R_1 + \frac{R_{23}R_4}{R_{23} + R_4} = R_1 + \frac{(R_2 + R_3)R_4}{R_2 + R_3 + R_4}$$

However, this more complicated expression is a bit unwieldy and it does not add much to our understanding of R_{eq} . In a problem in which numerical values of R_1 , R_2 , R_3 and R_4 are specified, it would be less cumbersome to substitute the numerical values into the formulas for R_{23} and R_{234} at this stage, and then use the numerical value of R_{eq} in subsequent computations.

Step 2: Compute the total current leaving the battery.

Ohm's law for the equivalent circuit is

$$V_b = I_{\text{tot}} R_{\text{eq}}$$

Therefore, since V_b and R_{eq} are known

$$I_{\text{tot}} = \frac{V_b}{R_{\text{eq}}}.$$

This concludes part (a) of this problem. Note that part (b) and part (c) of this problem are the same as part (b) and part (c) of the preceding problem.

- b. The power dissipated by the entire circuit can be computed from any of these formulas.

$$P_{\text{tot}} = I_{\text{tot}}^2 R_{\text{eq}} \quad \text{or} \quad P_{\text{tot}} = V_b I_{\text{tot}} \quad \text{or} \quad P_{\text{tot}} = \frac{V_b^2}{R_{\text{eq}}}.$$

From the givens, V_b and all the resistance values are known. From the analysis of part (a), R_{eq} is known. Thus, at this point in the analysis, all three of the formulas can be computed directly.

- c. The power dissipated by R_1 can be computed from any one of these formulas


$$P_1 = I_1^2 R_1 \quad \text{or} \quad P_1 = V_1 I_1 \quad \text{or} \quad P_1 = \frac{V_1^2}{R_1}.$$

Note that additional work would be required to find V_1 . Since R_1 is in series with the battery,

$$I_1 = I_{\text{tot}} \quad \text{therefore,} \quad P_1 = I_{\text{tot}}^2 R_1$$

————— \diamond —————

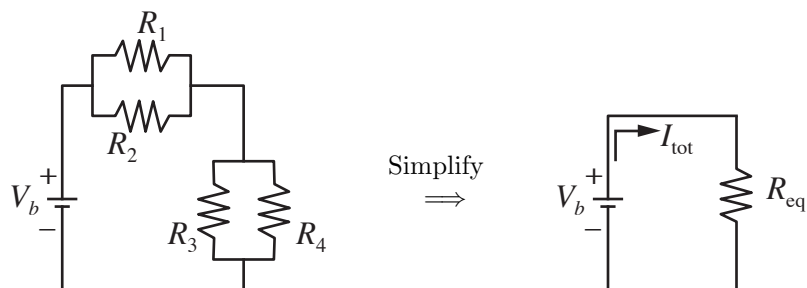3. The circuit to be analyzed is shown below left. The first step of the analysis is to compute R_{eq} to obtain the equivalent circuit to the right.



The steps are the same as in the preceding exercise. However, since the arrangement of resistances is different, the formula for R_{eq} will be different.

- a. Compute the total current supplied by the battery.

Step 1: Obtain a formula for the equivalent resistance, R_{eq} of the entire circuit.

R_1 and R_2 are in parallel and can be combined into an equivalent resistance R_{12}



$$\frac{1}{R_{12}} = \frac{1}{R_1} + \frac{1}{R_2} \quad \text{or} \quad R_{12} = \frac{R_1 R_2}{R_1 + R_2}$$

Similarly, R_3 and R_4 are in parallel and can be combined into an equivalent resistance R_{34}

$$\frac{1}{R_{34}} = \frac{1}{R_3} + \frac{1}{R_4} \quad \text{or} \quad R_{34} = \frac{R_3 R_4}{R_3 + R_4}$$

R_{12} and R_{34} are in series and can be combined into an equivalent resistance R_{1234} . Since R_{1234} is the only remaining resistance, it is also R_{eq} for the entire circuit, i.e., $R_{1234} = R_{\text{eq}}$.
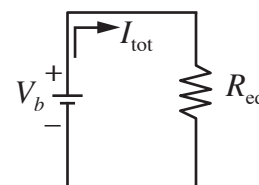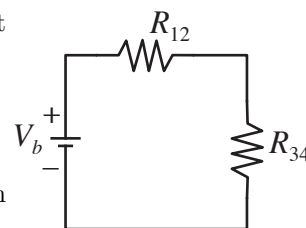
$$R_{1234} = R_{\text{eq}} = R_{12} + R_{34}$$



We can substitute the definitions of R_{12} and R_{34} into the expression for R_{eq} to get

$$R_{\text{eq}} = \frac{R_1 R_2}{R_1 + R_2} + \frac{R_3 R_4}{R_3 + R_4}$$

Once again, this slightly unwieldy formula is not more instructive than the equivalent form, $R_{\text{eq}} = R_{12} + R_{34}$. At this point in an analysis with known values for R_1 , R_2 , R_3 and R_4 , it would be better to substitute those values into the formula for R_{eq} , and then treat R_{eq} as a known numerical value.

Step 2: Compute the total current leaving the battery.

Ohm's law for the equivalent circuit is

$$V_b = I_{\text{tot}} R_{\text{eq}}$$

Therefore, since V_b and R_{eq} are known

$$I_{\text{tot}} = \frac{V_b}{R_{\text{eq}}}$$

This concludes part (a) of this problem. Note that part (b) of this problem are the same as part (b) of the preceding problem. Part (c) requires some additional analysis

- b. The power dissipated by the entire circuit can be computed from any of these formulas.

$$P_{\text{tot}} = I_{\text{tot}}^2 R_{\text{eq}} \quad \text{or} \quad P_{\text{tot}} = V_b I_{\text{tot}} \quad \text{or} \quad P_{\text{tot}} = \frac{V_b^2}{R_{\text{eq}}}.$$


From the givens, V_b and all the resistance values are known. From the analysis of part (a), R_{eq} is known. Thus, at this point in the analysis, all three of the formulas can be computed directly.

- c. The power dissipated by R_1 can be computed from one of these formulas.

$$P_1 = I_1^2 R_1 \quad \text{or} \quad P_1 = V_1 I_1 \quad \text{or} \quad P_1 = \frac{V_1^2}{R_1}.$$

At this point in the analysis, only the given value of R_1 is known. Calculation of V_1 or I_1 will require additional effort. Note that if V_1 was known, it would be easy to compute I_1 from Ohm's law, viz., $I_1 = V_1/R_1$. However, if V_1 was known, it would quicker to directly compute $P_1 = V_1^2/R_1$. We will use Kirchoff's voltage law to find V_1 .

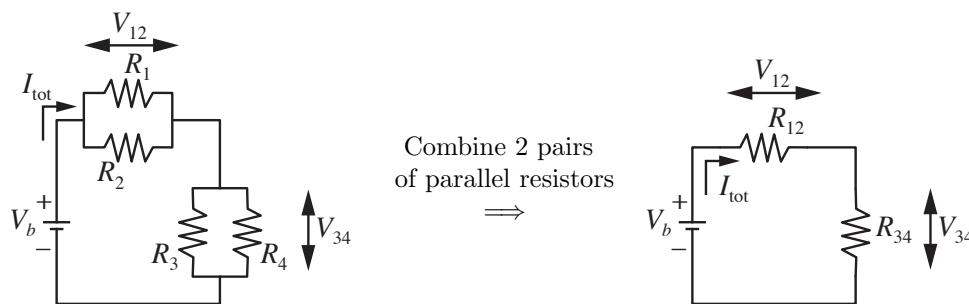Below left is the original circuit diagram with identification of the voltage drops V_{12} and V_{34} , and the total current leaving the battery, I_{tot} . Below right is the same circuit after one degree of simplification that was achieved by combining R_1 and R_2 into the equivalent resistance R_{12} , and by combining R_3 and R_4 into the equivalent resistance R_{34} .



Because R_1 and R_2 are in parallel, the voltage drop, V_{12} is the same as the voltage drop for R_1 and for R_2 .

$$V_{12} = V_1 = V_2$$

Therefore, (for this circuit!), by finding V_{12} we will know V_1 .

From the preceding analysis, $I_{\text{tot}} = V_b/R_{\text{eq}}$ is known. Applying Ohm's law to the equivalent resistance R_{12} gives

$$V_{12} = I_{\text{tot}} R_{12}$$

Since I_{tot} and R_{12} are known, the preceding formula gives the value for V_{12} . Therefore

$$P_1 = \frac{V_1^2}{R_1} = \frac{V_{12}^2}{R_1} = \frac{(I_{\text{tot}} R_{12})^2}{R_1}$$

The terms in the last expression on the right hand side are computable from the given constants of the problem (V_b , R_1 , R_2 , R_3 and R_4).

————— \diamond —————