

# ME 120

## Practice problems: compute V, I, P in simple circuits


For all the problems shown below:

- $R_i$  is the resistor number  $i$ , with  $i=1, 2, 3\dots$
- $R_{eq}$  is the equivalent resistor of the whole circuit
- $V_i$  is the voltage across each resistor
- $V_s$  is the voltage supplied by the battery (or voltage supply)
- $I_i$  is the current going through each resistor
- $I$  is the current leaving the battery
- $P_i$  is the power dissipated by each resistor
- $P_s$  is the power generated by the battery. Whatever the circuit, we always have:  $P_s = \sum P_i$

Compute V, I, P for each component of each circuit **as a function of  $V_s$  and the resistors  $R_i$** .

Hint: To compute the power in a timely manner, although  $P_i = V_i \cdot I_i$  you only need to calculate either  $V_i$  or  $I_i$  (whatever is the easiest), as the power can also be expressed as:  $P_i = R_i \cdot I_i^2$  or  $P_i = \frac{V_i^2}{R_i}$  using Ohm's law and substituting in the equation.

## 1. 2 resistors in series

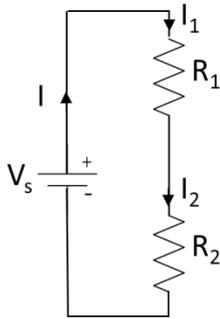

$$R_{eq} = R_1 + R_2$$

a) Let's compute the current through each component:

First, let's find  $I$ . We need to express the current as a function of  $V_s$  and the resistors  $R_i$ . Using Ohm's law across the battery,  $V_s = R_{eq} \cdot I$

$$\text{Therefore } I = \frac{V_s}{R_{eq}} = \frac{V_s}{R_1 + R_2}$$

$$I = I_1 = I_2. \text{ Therefore } I_1 = I_2 = \frac{V_s}{R_1 + R_2}$$

b) Let's compute the voltage across each component:

We already have  $V_s$ , as it is a given. Now, to find  $V_i$  across each resistor:

Using Ohm's law for each resistor ( $V_i = R_i \cdot I_i$ ) and substituting for  $I_i$  using the equation in a), we have:

$$V_1 = R_1 \cdot I_1 = R_1 \cdot I = R_1 \cdot \frac{V_s}{R_1 + R_2} \text{ and}$$

$$V_2 = R_2 \cdot I_2 = R_2 \cdot I = R_2 \cdot \frac{V_s}{R_1 + R_2}$$

We can check that we have Kirchoff's voltage law:  $V_s = V_1 + V_2$

c) Let's compute the power generated by the battery and the power dissipated by each component:

$$\text{Power generated by the battery: } P_s = V_s \cdot I = V_s \cdot \frac{V_s}{R_1 + R_2} = \frac{V_s^2}{R_1 + R_2}$$

Power dissipated by each resistor:

We can express the power for each resistor in different ways using  $P=VI$  and  $V=RI$ .


$$\text{For } R_1: P_1 = V_1 \cdot I_1 = R_1 \cdot I_1^2 = R_1 \cdot I^2$$

$$\text{We have already computed } I, \text{ and we find: } P_1 = R_1 \cdot \left( \frac{V_s}{R_1 + R_2} \right)^2.$$

$$\text{Using the same logic, } P_2 = R_2 \cdot \left( \frac{V_s}{R_1 + R_2} \right)^2.$$

We can now verify that  $P_s = P_1 + P_2$

## 2. 2 resistors in parallel

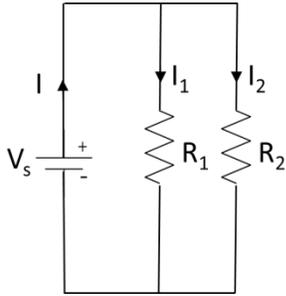

$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{R_1 \cdot R_2}{R_1 + R_2}$$

a) Let's compute the voltage across each component:

$$V_s = V_1 = V_2$$

b) Let's compute the current through each component:

For the resistors, using Ohm's law for each component ( $I_i = \frac{V_i}{R_i}$ ) and substituting for  $V_i$  using the equation in a), we have:

$$I_1 = \frac{V_1}{R_1} = \frac{V_s}{R_1}$$

$$I_2 = \frac{V_2}{R_2} = \frac{V_s}{R_2}$$

$$\text{For the battery: } I = \frac{V_s}{R_{eq}} = V_s \cdot \frac{R_1 + R_2}{R_1 \cdot R_2} = V_s \cdot \left( \frac{1}{R_2} + \frac{1}{R_1} \right)$$

We can check that we have Kirchoff's current law:  $I = I_1 + I_2$

c) Let's compute the power generated by the battery and the power dissipated by each component:

$$\text{Power generated by the battery: } P_s = V_s \cdot I = V_s \cdot V_s \cdot \left( \frac{1}{R_2} + \frac{1}{R_1} \right) = V_s^2 \cdot \left( \frac{1}{R_2} + \frac{1}{R_1} \right)$$

Power dissipated by each resistor:


We can express the power for each resistor in different ways using  $P=VI$  and  $V=RI$ .

$$\text{For } R_1: P_1 = V_1 \cdot I_1 = \frac{V_1^2}{R_1} = \frac{V_s^2}{R_1}$$

$$\text{Using the same logic, } P_2 = V_2 \cdot I_2 = \frac{V_2^2}{R_2} = \frac{V_s^2}{R_2} .$$

We can now verify that  $P_s = P_1 + P_2$

### 3. 3 resistors in series

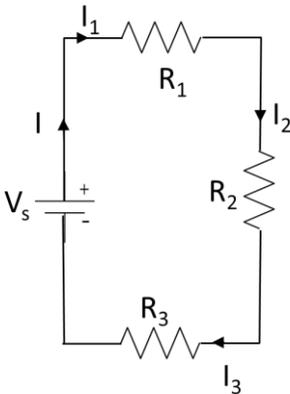

$$R_{eq} = R_1 + R_2 + R_3$$

a) Let's compute the current through each component:

First, let's find \$I\$. We need to express the current as a function of \$V\_s\$ and the resistors \$R\_i\$. Using Ohm's law across the battery,  $V_s = R_{eq} \cdot I$

$$\text{Therefore } I = \frac{V_s}{R_{eq}} = \frac{V_s}{R_1 + R_2 + R_3}$$

$$I = I_1 = I_2 = I_3. \text{ Therefore } I_1 = I_2 = I_3 = \frac{V_s}{R_1 + R_2 + R_3}$$

b) Let's compute the voltage across each component:

We already have \$V\_s\$, as it is a given. Now, to find \$V\_i\$ across each resistor:

Using Ohm's law for each resistor ( $V_i = R_i \cdot I_i$ ) and substituting for \$I\_i\$ using the equation in a), we have:

$$V_1 = R_1 \cdot I_1 = R_1 \cdot I = R_1 \cdot \frac{V_s}{R_1 + R_2 + R_3}$$

$$V_2 = R_2 \cdot I_2 = R_2 \cdot I = R_2 \cdot \frac{V_s}{R_1 + R_2 + R_3}$$

$$V_3 = R_3 \cdot I_3 = R_3 \cdot I = R_3 \cdot \frac{V_s}{R_1 + R_2 + R_3}$$

We can check that we have Kirchoff's voltage law:  $V_s = V_1 + V_2 + V_3$

c) Let's compute the power generated by the battery and the power dissipated by each component:

$$\text{Power generated by the battery: } P_s = V_s \cdot I = V_s \cdot \frac{V_s}{R_1 + R_2 + R_3} = \frac{V_s^2}{R_1 + R_2 + R_3}$$

Power dissipated by each resistor:

We can express the power for each resistor in different ways using  $P=VI$  and  $V=RI$ .


$$\text{For } R_1: P_1 = V_1 \cdot I_1 = R_1 \cdot I_1^2 = R_1 \cdot I^2$$

$$\text{We have already computed } I, \text{ and we find: } P_1 = R_1 \cdot \left( \frac{V_s}{R_1 + R_2 + R_3} \right)^2$$

$$\text{Using the same logic, } P_2 = R_2 \cdot \left( \frac{V_s}{R_1 + R_2 + R_3} \right)^2 \text{ and } P_3 = R_3 \cdot \left( \frac{V_s}{R_1 + R_2 + R_3} \right)^2$$

We can now verify that  $P_s = P_1 + P_2 + P_3$

## 4. 3 resistors in parallel

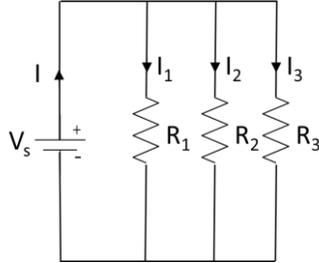

$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$

a) Let's compute the voltage across each component:

$$V_s = V_1 = V_2 = V_3$$

b) Let's compute the current through each component:

For the resistors, using Ohm's law for each component ( $I_i = \frac{V_i}{R_i}$ ) and substituting for  $V_i$  using the equation in a), we have:

$$I_1 = \frac{V_1}{R_1} = \frac{V_s}{R_1}$$

$$I_2 = \frac{V_2}{R_2} = \frac{V_s}{R_2}$$

$$I_3 = \frac{V_3}{R_3} = \frac{V_s}{R_3}$$

$$\text{For the battery: } I = \frac{V_s}{R_{eq}} = V_s \cdot \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$

We can check that we have Kirchoff's current law:  $I = I_1 + I_2 + I_3$

c) Let's compute the power generated by the battery and the power dissipated by each component:

$$\text{Power generated by the battery: } P_s = V_s \cdot I = V_s \cdot V_s \cdot \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) = V_s^2 \cdot \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$

Power dissipated by each resistor:

We can express the power for each resistor in different ways using  $P=VI$  and  $V=RI$ .

$$\text{For } R_1: P_1 = V_1 \cdot I_1 = \frac{V_1^2}{R_1} = \frac{V_s^2}{R_1}$$

$$\text{Using the same logic, } P_2 = \frac{V_s^2}{R_2} \text{ and } P_3 = \frac{V_s^2}{R_3}$$

We can now verify that  $P_s = P_1 + P_2 + P_3$